

Lab 9 – Notes

Fall 2023

JOHN GERGUIS

General Notes

- Lab 9 is an extra credit lab that you can do if you would like to get a bump to your grade.
- You can do the prelab 9 or/and the report 9.
- The submissions on gradescope are open till the end of the semester.

Prelab

Task 9.4.1: Prelab Questions

1. Calculate the step response $v_C(t)$ for $t > 0$ for the circuit in figure 9.10.

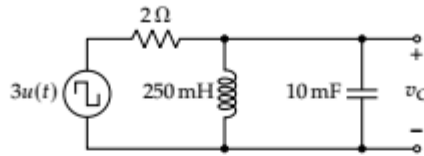


Figure 9.10: Parallel RLC Circuit

2. Calculate the Thévenin equivalent resistance shown in figure 9.11 by solving for the ratio $v_{\text{test}}/i_{\text{test}}$.

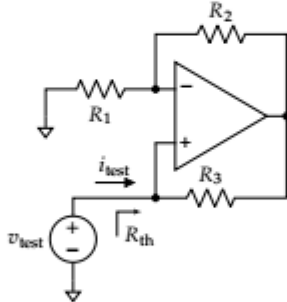


Figure 9.11: A negative impedance converter circuit

3. Plot the first $200\ \mu\text{s}$ of $v_C(t)$ in figure 9.12 if $v_C(0) = 1\text{ mV}$ and $i_L(0) = 0$ using Python's NumPy, MATLAB®, or a similar plotting tool.

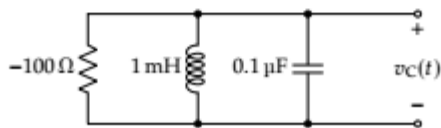


Figure 9.12: A parallel RLC circuit

1. You can solve either using Laplace or using the procedure in the solved examples, you don't need to start from the differential equations, just use the summary of relations (section 9.3.1).

2. This introduces the concept of negative resistance which you will be using in task 3.

3. Solve by the same way as problem 1 to get $V_C(t)$. Make sure to use $-100\ \Omega$ (negative value). Plot $V_C(t)$ on Matlab for example for $t:0-200\ \mu\text{s}$.

Task 1

Task 9.5.1: Series RLC response measurements

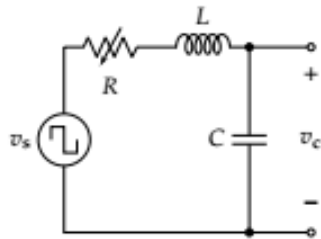


Figure 9.13: A series RLC circuit.

For this task, use $L = 1 \text{ mH}$ and $C = 0.001 \text{ }\mu\text{F}$. Assume zero initial conditions. Even though the input square wave is a time varying signal, if the period is much longer than the response, then it is effectively constant. One half of the square wave sets the initial conditions, and the other half provides a constant input.

1. Let v_s be a square wave that varies between 0 V and 3 V at 1 kHz. Adjust the potentiometer R to obtain and capture an underdamped and overdamped v_c response.

2. Calculate the peak to peak value of v_s and a resistance value^a to obtain the response

$$v_c(t) = 3.5e^{-1.558 \times 10^6 t} - 8.5e^{-642 \times 10^3 t} + 4$$


3. Replace the potentiometer with the fixed resistor computed in the last step. Capture the waveform v_c by applying the correct input and downloading the data from the oscilloscope.
4. Use Python's NumPy or MATLAB®, to plot and compare data collected from the oscilloscope with the expected response.

^a Hint: compute $s_1 + s_2$ using equation (9.10).

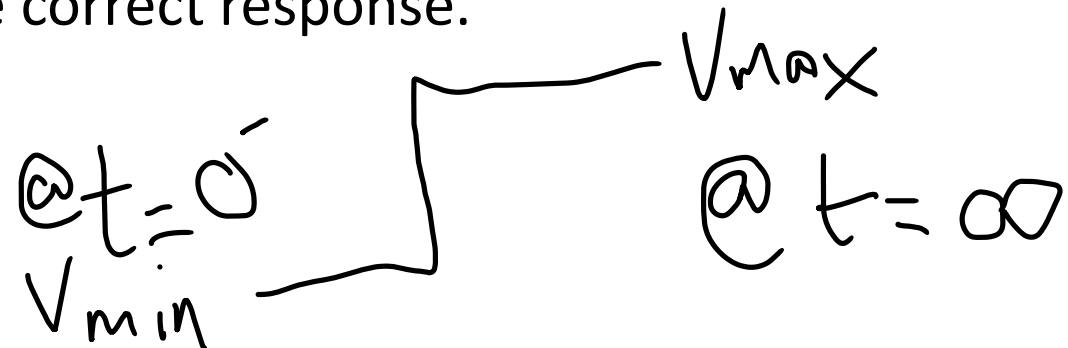1. Tune the potentiometer and take screenshots for underdamped and overdamped responses.



- 2/3. You will need to compute V_{\min} and V_{\max} of the required square wave & the value of R first. Then you need to put input square wave from the wavegen with those values and place that R to get the correct response.



4. Extract the measured data and plot it over the relation of $V_c(t)$ given in step 2, they should be very close to each other.

Task 2

Task 9.5.2: Parallel RLC response measurements

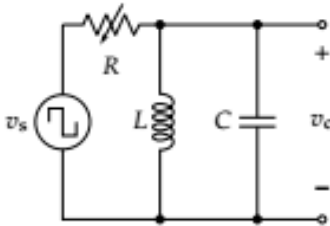


Figure 9.14: A parallel RLC circuit.


For this task, use $L = 1 \text{ mH}$ and $C = 2 \text{ nF}$. Assume zero initial conditions. Even though the input square wave is a time varying signal, if the period is much longer than the response, then it is approximately constant. One half of the square wave sets the initial conditions and the other half provides a constant input.

1. Let v_s be a square wave that varies between 0 V and 3 V at 1 kHz. Adjust the potentiometer R to obtain and capture an underdamped and overdamped v_c response.
2. Determine the peak value of v_s and compute a resistance value to obtain the response

$$v_c(t) = 1.3e^{-9.2 \times 10^4 t} (\sin 7 \times 10^5 t)$$

3. Replace the potentiometer with the fixed resistor computed in the last step. Capture the waveform v_c by applying the correct input and downloading the data from the scope.
4. Use Python's NumPy or MATLAB® to plot and compare data collected from the oscilloscope with the expected response.

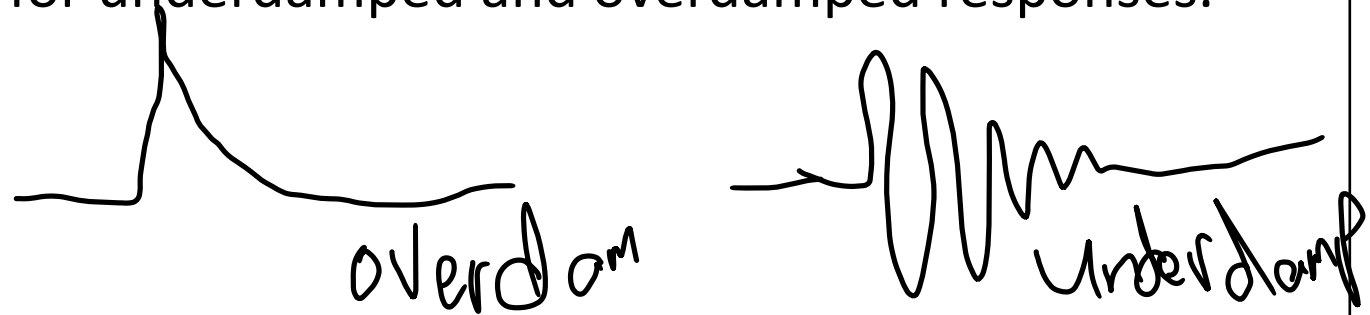1. Tune the potentiometer and take screenshots for underdamped and overdamped responses.



- 2/3. You will need to compute V_{\max} of the required square wave & the value of R first. Then you need to put input square wave from the wavegen with those values and place that R to get the correct response.

$$V_{\min} = 0$$

$$V_c(0) = \frac{V_{\max}}{2}$$

4. Extract the measured data and plot it over the relation of $V_c(t)$ given in step 2, they should be very close to each other.

Task 3

Task 9.5.3: Oscillator

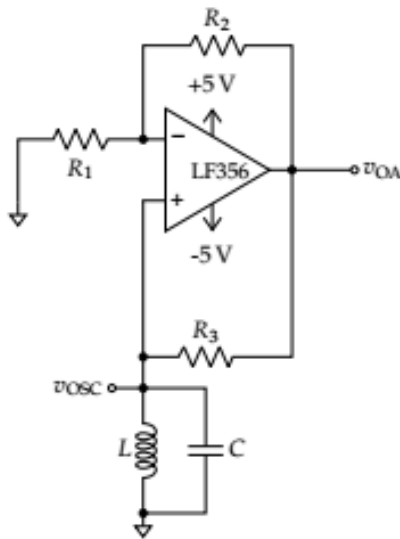


Figure 9.15: An oscillator circuit.

For this task, use $R_1 = R_2 = 1 \text{ k}\Omega$, $R_3 = 100 \Omega$, $L = 1 \text{ mH}$, and $C = 0.1 \mu\text{F}$.

1. Measure the ESR of the inductor.
2. Simulate the circuit in figure 9.15. Use the measured ESR values for the inductor. Obtain plots of v_{OA} and v_{OSC} .
3. Construct the oscillator circuit.
4. Capture an oscilloscope screenshot showing v_{OUT} and v_{OSC} with frequency and peak to peak measurements.
5. Calculate the error between the simulated frequency and measured frequency. How do these relate to ω_d for the circuit?

1. You can measure the ESR (equivalent series resistance) by the AD2 using the Impedance Analyzer tool and use a series resistance of 100Ω . Of course, you can use the ohmmeter or the DMM if you have.

2. Simulate the whole circuit on LT spice (check the guide on Brightspace). Please use the following link to download the opamp model:

<https://www.ti.com/lit/zip/snom255>

3/4. Build the circuit and measure it. Note that the circuit is an oscillator which oscillates on its own (i.e. just needs the +/- 5v supplies).

5. Compute the oscillation frequency from the relation below, and compute it from the measurements and simulations. Compare the 3 values.

$$\omega_d = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2} \quad (\text{Parallel})$$

Note that $f_d = \frac{\omega_d}{2\pi}$, and R is value of the negative resistance (use the relation that you have derived in the perlab problem 2).