


Prelab 3

Wednesday, September 4, 2024 23:04

Curve tracer Overview

general concept

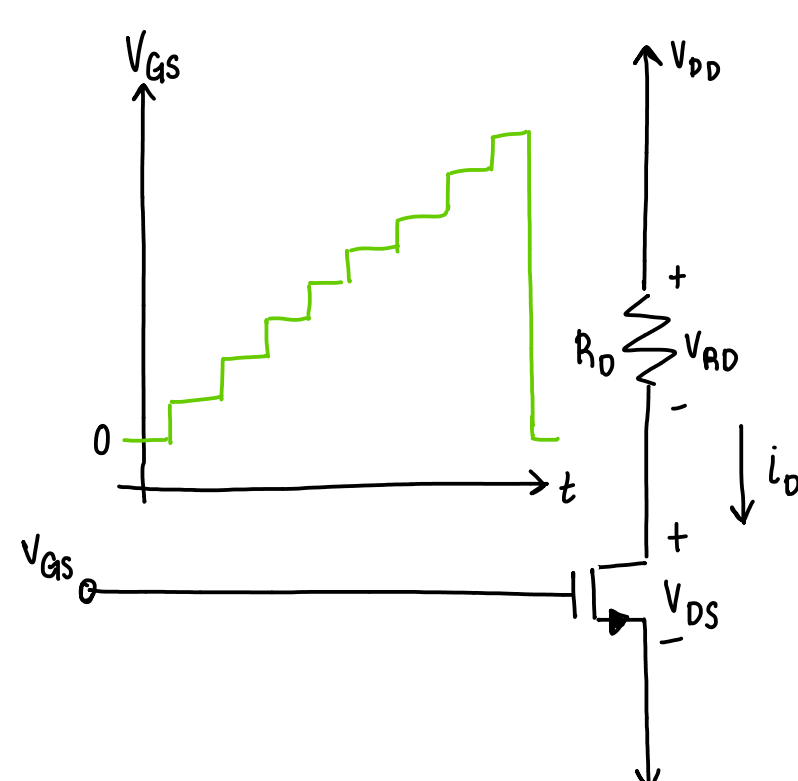- starts by setting $V_{GS} = 0$
- V_{DS} swept from 0 to V_{DD} {producing 1 trace}
- V_{GS} stepped by a constant amount
 - repeated until reaches maximum V_{GS}
- ° starts over again at $V_{GS} = 0$
 - endlessly repeats process



curve tracer concept

Small signal transconductance

- small signal parameter used to describe behavior of a device near a certain bias point


$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

to estimate from a curve tracer:

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Threshold voltage tester

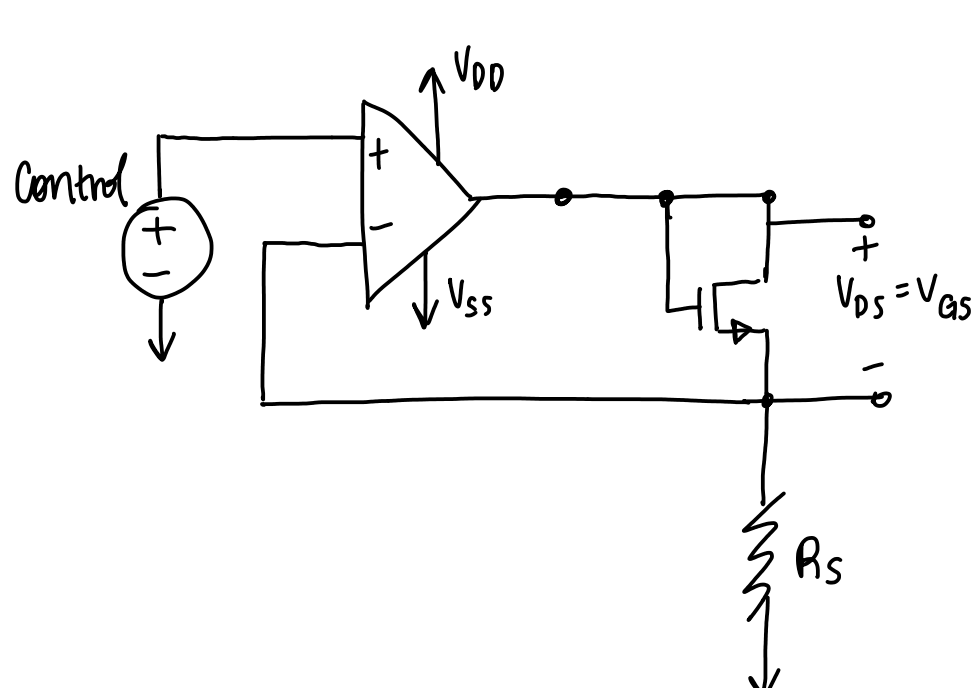- can build simple op-amp circuit to automatically bias the transistor to V_{th}
 - makes measuring V_{th} very simple



automatic threshold voltage tester

- forces $V_{DS} = V_{GS}$ by connecting Gate & Drain
 - automatically sets voltage @ Drain & gate node to desired I_D
 - I_D programmed by changing $V_{control}$ and R_S

Measured Value of $V_{GS} = \text{threshold voltage of device}$

- ° opamp ensures correct amount of current flowing

Prelab 3.6.1

° N-channel MOSFET

$$V_{th} = 1V$$

$$V_{GS} = 1.5V$$

$$I_D = 10mA$$

what is K_n ?

$$K = \frac{2 I_D}{(V_{GS} - V_{th})^2} = \frac{20}{(1.5 - 1)^2} = 80$$

$$K_n = 80$$

use 3.3 & 3.4 to calculate the ideal value of g_m in terms of V_{GS} , K_n , V_{th}

$$I_D = \frac{K_n}{2} (V_{GS} - V_{th})^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$y = \frac{C_1}{2} (x - c_2)^2$$


$$\frac{C_1}{2} 2(x - c_2) = 1$$

$$I_D = \frac{2 K_n}{2} (V_{GS} - V_{th}) = g_m$$

$$g_m = K_n (V_{GS} - V_{th})$$

Virtual short circuit analysis on the circuit 3.2

to find I_D in terms of R_S & V_{ctrl}

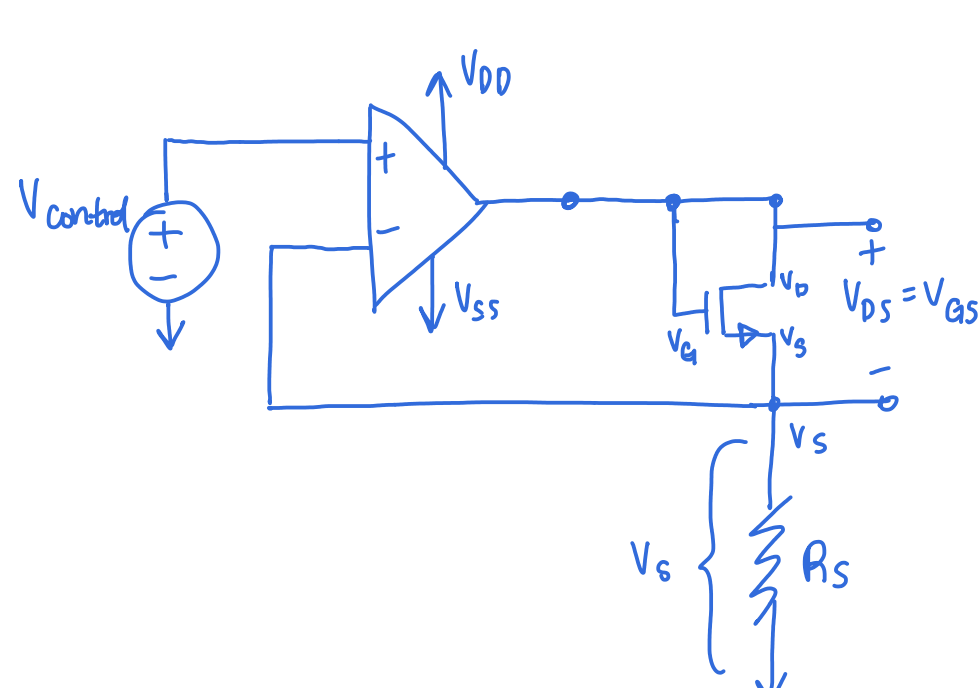

assuming $V_+ \& V_-$ same

MAKES $V_{control} = V_D$

Voltage drop across $R_S = V_S$

$V_S = V_{control} \rightarrow \text{makes } V_D = V_S$

$$I_D = \frac{V_S}{R_S}$$

$$I_D = \frac{V_{control}}{R_S}$$

$R_S = 100k$ what should $V_{control}$ be for I_D to be $1\mu A$

$$1\mu A = \frac{V_{ctrl}}{100k\Omega} \Rightarrow 0.1 = V_{ctrl}$$