

# MOSFET Differential Amplifier with Current Mirror

## 5.1 Application

In practical terms one of the many useful applications of a differential amplifier is in noise resistant circuits. Consider that all electrical circuits require two conduction paths—an outgoing ( $a$ ) and return ( $b$ ) path. The signal ( $y$ ) is the voltage difference between them, thus

$$y = a - b$$

If a noise signal ( $N$ ) couples onto those conductors, it will produce a similar change on both:

$$y = (a + N) - (b + N)$$

If the receiver design is based on a differential amplifier, it will amplify the difference while rejecting the noise, which allows for reconstructing the original signal:

$$y = (a + N) - (b + N)$$

$$y = a + N - b - N$$

$$y = a - b$$

Most modern digital communication systems use differential amplifiers in their receivers: memory, CPU to CPU, and PCIe buses, HDMI, USB, Thunderbolt, Ethernet, and many more. Differential amplifiers also serve as the input stage to operational amplifiers (op amps), which form the basis of most modern analog circuits.



**Figure 5.1:** Four twisted pairs are used in CAT6 ethernet cable to carry differential signals. This allows for sending data long distances through potentially electrically noisy environments.

## 5.2 Background

If we consider the two-port circuits we have studied so far, they have a significant limitation: their output depends on a single input. In mathematics, any operation that acts on only one variable is called a *unary* operator, e.g.,  $\sin(x)$ . To create useful systems, *binary* operators that act on two inputs are essential.

This lab focuses on the basic building block of the majority of real-world amplifiers and signal processing systems, the differential amplifier.<sup>(1)</sup>


Differential amplifiers are widely used in modern analog and digital design. For example, they are typically the first stage of the ubiquitous op amp device. In fact, the MOSFET differential amplifier will be developed into a two-stage op amp in experiment 6.

This experiment investigates the MOSFET based differential amplifier with current source biasing. The entire circuit can be found in figure 5.9.

In case you have not realized it yet,  $y = a + b$  and  $y = a - b$  are examples of binary operators. Without a binary circuit a designer cannot add, subtract, multiply, etc.

<sup>(1)</sup> The simplest useful differential amplifier circuits are called the “differential pair” when built from bipolar junction transistors (BJTs) or the “source-coupled differential pair” when built from metal-oxide-semiconductor field-effect transistors (MOSFETs), however, both are very similar.

## 5.3 The differential amplifier

 

**Figure 5.2:** Schematic symbol for a differential amplifier.

As seen in figure 5.2, the differential amplifier is a three-terminal device. Terminals  $v_{IN}^-$  and  $v_{IN}^+$  are inputs and  $v_{OUT}$  is the amplifier’s output.

The first-order function of the ideal differential amplifier is to sense the voltage at each input, subtract them and multiply the result by a gain. In other words, the input-output characteristic is given by the following:

$$v_{OUT} = A_d (v_{IN}^+ - v_{IN}^-) \quad (5.1)$$

A differential amplifier can easily be confused with an op amp; however, there are noteworthy differences. Experiment 6 explores MOSFET op amps in depth, so for now note that differential amplifiers are only the first stage of most modern op amps.

### 5.3.1 Differential versus common mode input

Unfortunately, real differential amplifiers are non-ideal. To study the non-idealities it is helpful to break the input signal into two separate parts: the so-called differential and common mode components. We then use superposition to analyze the system’s response to each part separately.

### The differential input, $v_d$

We have already seen the differential input  $v_d$ . It is simply the difference between the two inputs  $v_{IN}^+$  and  $v_{IN}^-$ ; that is,

$$v_d = v_{IN}^+ - v_{IN}^- \quad (5.2)$$

### The common mode input, $v_{cm}$

The common mode input  $v_{cm}$  is the average of the input signals  $v_{IN}^+$  and  $v_{IN}^-$ ; that is:

$$v_{cm} = \frac{1}{2}(v_{IN}^+ + v_{IN}^-) \quad (5.3)$$

In other words, the common mode input is the shared voltage between the two signals. By virtue of the subtraction in equation (5.1), this is the portion of the input that differential amplifier will reject, or, in other words, cancel out and not amplify.

It is sometimes useful to define  $v_{IN}^+$  and  $v_{IN}^-$  in terms of their differential and common mode parts. The definition is as follows:

$$\begin{aligned} v_{IN}^- &= v_{cm} - \frac{v_d}{2} \\ v_{IN}^+ &= v_{cm} + \frac{v_d}{2} \end{aligned}$$

### 5.3.2 The non-ideal differential amplifier

Reformulating equation (5.1) by splitting the input and gain terms into their differential ( $v_d, A_d$ ) and common mode ( $v_{cm}, A_{cm}$ ) forms results in the following input-output relationship:

$$v_{OUT} = A_d v_d + A_{cm} v_{cm} \quad (5.4)$$

Reasonably well-designed differential amplifiers will have an  $A_{cm}$  that is many orders of magnitude smaller than  $A_d$ . None the less, we include the common mode term to ensure a thorough analysis. In practice, non-zero common mode gain can result from mismatches in the transistors and other circuit components.<sup>(2)</sup>

An ideal differential amplifier has  $A_{cm} = 0$  so equation (5.4) reduces to equation (5.1)

$$v_{OUT} = A_d v_d.$$

<sup>(2)</sup> Advancements in analog integrated circuit (IC) fabrication such as laser trimming and fuse arrays have significantly improved common mode rejection in many off the shelf amplifiers.

### 5.3.3 Measuring the performance of a differential amplifier: Common mode rejection ratio

The main figure of merit for measuring the quality of a differential amplifier is to compare the magnitude of the differential and common mode gains. To do so, one can use the common mode rejection ratio (CMRR) metric. That is, the ratio of the differential gain to common-mode gain:

$$CMRR \equiv \frac{|A_d|}{|A_{cm}|}$$

Because well-designed differential amplifiers will have very large common mode rejection ratios, it is often expressed in decibels of power<sup>(3)</sup>

<sup>(3)</sup> Conversion from voltage gain to power gain is done assuming the input resistance is the same as the load resistance. Thus,

$$\begin{aligned} \frac{P_{out}}{P_{in}} &= \frac{v_{out}^2/R_{load}}{v_{in}^2/R_{in}} \\ \frac{P_{out}}{P_{in}} &= \frac{v_{out}^2}{v_{in}^2} \\ \frac{P_{out}}{P_{in}} &= \left( \frac{v_{out}}{v_{in}} \right)^2 = A_V^2 \end{aligned}$$

Note that this makes the unit of measurement watts, not volts!


$$\text{CMRR (dB)} \equiv 20 \log \frac{|A_d|}{|A_{cm}|} \quad (5.5)$$

The INA226 [1], a current and power monitor IC from Texas Instruments, has a minimum CMRR of 166 dB. Even the LM358 [2] op amp released in 1976 has a CMRR of 80 dB.

## 5.4 Differential amplifier

Now that we have introduced the basic concepts of a differential amplifier, let us take a turn to the practical side and consider the actual design in figure 5.3. At the core of the circuit structure is a MOSFET matched pair<sup>(4)</sup> made from  $Q_1$  and  $Q_2$  biased by a constant current source. As was done in experiment 4, we will use a current mirror to realize the current source. For the moment, we will assume the current mirror has a nearly infinite output impedance. Finally, the amplifier is loaded with equal resistors  $R_D$ .

<sup>(4)</sup> By a matched pair we mean the two transistors with nearly equal parameters ( $k'$ ,  $\frac{W}{L}$ , and  $V_{th}$ )

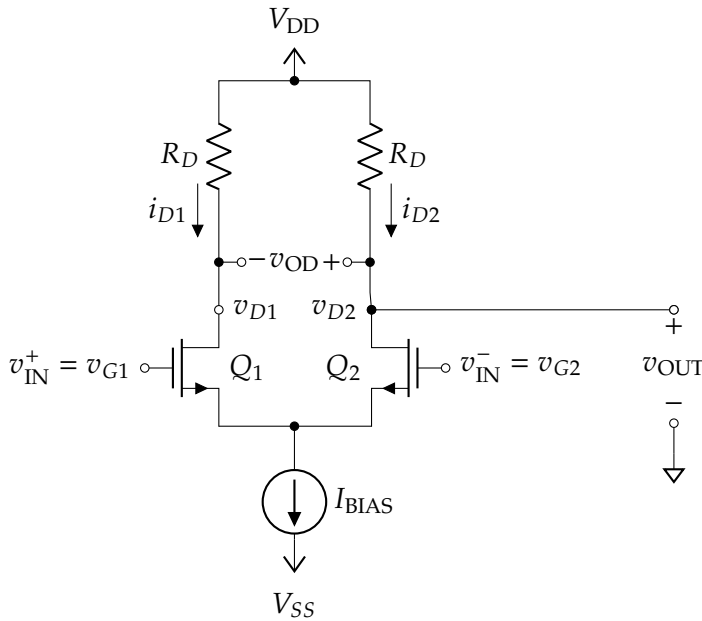

**Figure 5.3:** N-channel MOSFET (NMOS) differential amplifier with current source bias.

### 5.4.1 Large signal analysis

We begin by reminding ourselves that, when in the saturation region, the current through the drains of the two MOSFETs in figure 5.3 are equal to

$$i_{D1} = \frac{1}{2} k' \frac{W}{L} (v_{GS1} - V_{th})^2 \quad (5.6)$$

and

$$i_{D2} = \frac{1}{2} k' \frac{W}{L} (v_{GS2} - V_{th})^2 \quad (5.7)$$

It is worth noting that the analysis in this section applies to both AC and DC inputs and does not require any assumptions of small signal. However, we are using the equations of a MOSFET in saturation, so we do have to be careful to ensure they are all operating somewhere in that region.

Next, we apply Kirchoff's current law at the source network of  $Q_1$  and  $Q_2$  and arrive at the equation we will use to calculate the operation of the differential amplifier

$$i_{D1} + i_{D2} = I_{BIAS} \quad (5.8)$$

This relationship says that under all circumstances the current  $I_{BIAS}$  must split itself between the two branches of the differential pair.

### Amplifier output due to common mode input

To get started, we consider how the circuit responds to a common mode input. First, we note that a signal composed entirely of common mode voltage results in  $v_{G1} = v_{G2}$ . Therefore, because  $Q_1$  and  $Q_2$  are matched, we will find that equation (5.6) and equation (5.7) evaluate to the same current, so

$i_{D1} = i_{D2}$ . Combining this result with equation (5.8) leads to:

$$i_{D1} = i_{D2} = \frac{I_{BIAS}}{2}$$

Finally, we solve for  $v_{OUT}$  and find that:

$$v_{OUT} = V_{DD} - i_{D2}R_D = V_{DD} - \frac{I_{BIAS}}{2}R_D \quad (5.9)$$

Equation (5.9) shows that  $v_{OUT}$  is not affected by common mode inputs, as desired for an ideal differential amplifier.

As  $v_{GS}$  changes,  $i_D$  also changes; however, equation (5.9) shows the output is insensitive to common mode  $v_{GS}$ . This is a result of the current source  $I_{BIAS}$ .  $I_{BIAS}$  actively maintains a constant total current in the pair by adjusting the voltage dropped across itself. If a common mode increase in each transistor's gate voltages occurs, the current source will increase the voltage across it to ensure that  $v_{GS}$  never changes from its original value. This ensures that the original set current  $I_{BIAS}$  flows through the current source. This is one reason why a good current source is critical for quality common mode rejection.

### Current steering

From equation (5.8) we know that  $I_{BIAS}$  splits between the two drain currents and that common mode input results in an even split. Now we consider what happens when a differential voltage is applied.

Consider the case when  $v_{GS1} > v_{GS2}$ . From equation (5.6) and equation (5.7) we deduce that  $i_{D1} > i_{D2}$  because the transistors

If the parameters of a MOSFET are not matched, then an equal change in gate voltage can cause an unequal change in current while still satisfying equation (5.8). This results in a non-zero CMRR because some common mode input may "leak" into the output by virtue of the  $I_{BIAS}$  not perfectly splitting between the differential pair.

are matched. However, the sum of the drain currents must still equal  $I_{\text{BIAS}}$ , so  $i_{D2} = I_{\text{BIAS}} - i_{D1}$ .


By symmetry,  $i_{D2} > i_{D1}$  when  $v_{GS2} > v_{GS1}$ . The relative values of the gate-source voltage “steer” a proportional amount of current through the associated drain. As a result, the current flowing through each  $R_D$  changes which leads to a corresponding change in  $v_{\text{OUT}}$ .

### Small signal analysis: Voltage gain

As we continue our analysis of the differential amplifier, we need to find out how much it actually amplifies! We have seen that changing  $v_{GS1}$  and  $v_{GS2}$  relative to each other changes the current in each branch and therefore  $v_{\text{OUT}}$ . To completely understand the relationship, we convert figure 5.3 to its small signal equivalent, figure 5.4. Here, we assume that  $r_o$  is large enough that it can be safely ignored.<sup>(5)</sup>

Similar to the common mode case, the current source enforces a constant current by adjusting the voltage drop across its own leads. This adjustment is common to both transistors'  $v_{GS}$  which allows  $I_{\text{BIAS}}$  to remain constant even though the gate voltages may change.

<sup>(5)</sup> An assumption that should always be verified for a particular design.

 

**Figure 5.4:** Small signal model of the differential amplifier in figure 5.3, assuming  $r_o \gg R_D$

We proceed by leveraging superposition to simplify solving the circuit.<sup>(6)</sup> First, we look for a relationship between  $v_{\text{out}}$  and  $i_{d1}$  because we possess many tools to compute  $i_{d1}$ . We can use Ohm's law to find  $v_{\text{out}}$ :

$$v_{\text{out}} = -i_{d2}R_D = -g_m v_{gs2}R_D \quad (5.10)$$

Therefore, we must find an equation relating  $v_{gs2}$  and  $v_{\text{in}}^+$  so that it can be substituted into equation (5.10) and ultimately

<sup>(6)</sup> This is only possible because the small signal models of a MOSFET are composed of only linear circuit elements. These calculations will not hold if the MOSFET DC bias changes significantly.

worked into formula for gain, that is, the ratio  $v_{\text{out}}/v_{\text{in}}^+$ .

We start the super position argument by selecting  $v_{\text{in}}^+$  to be the input signal and grounding  $v_{\text{in}}^-$ , that is  $v_{\text{in}}^- = 0 \text{ V}$ . The following facts resulting from these choices will be helpful as we continue the analysis

$$v_{gs2} = v_{g2} - v_s = -v_s \quad (5.11)$$

$$v_{gs1} = v_{g1} - v_s = v_{\text{in}}^+ - v_s \quad (5.12)$$

Now we apply KCL by summing the currents feeding the source network, set them equal to zero, and simplify:

$$g_m v_{gs1} + g_m v_{gs2} = 0$$

$$v_{gs1} = -v_{gs2}$$

Using the observations from equation (5.11) and equation (5.12), we rewrite the last equation as:

$$v_{\text{in}}^+ - v_s = v_s$$

$$v_s = \frac{v_{\text{in}}^+}{2}$$

We recall that we are ultimately after an equation for  $v_{gs2}$  in terms of  $v_{\text{in}}^+$  and so return to equation (5.11) and arrive at

$$v_{gs2} = -\frac{v_{\text{in}}^+}{2}$$

Finally, we take equation (5.10) and replace  $v_{gs2}$  with the above result:

$$v_{\text{out},+} = \frac{1}{2} g_m R_D v_{\text{in}}^+ \quad (5.13)$$

One can work through a similar procedure to find  $v_{\text{out}}$  in terms of  $v_{\text{in}}^-$  when  $v_{\text{in}}^+$  is grounded. For the sake of brevity, we skip that derivation and jump directly to the final result, which is

$$v_{\text{out},-} = -\frac{1}{2} g_m R_D v_{\text{in}}^- \quad (5.14)$$

Now, we complete the superposition argument by adding each calculated  $v_{\text{out}}$ :


$$\begin{aligned} v_{\text{out}} &= v_{\text{out},+} + v_{\text{out},-} \\ v_{\text{out}} &= \frac{1}{2} g_m R_D v_{\text{in}}^+ - \frac{1}{2} g_m R_D v_{\text{in}}^- \\ v_{\text{out}} &= \frac{1}{2} g_m R_D (v_{\text{in}}^+ - v_{\text{in}}^-) = \frac{1}{2} g_m R_D v_d \end{aligned}$$

### Single-ended output gain

“Single ended output gain” refers to the gain when measuring only one of the differential amplifier outputs with respect to ground, which is just the value of  $v_{out}$  in ?? . We can compute the single-ended output gain as:

$$A_v = \frac{v_{out}}{v_d} = \frac{1}{2}g_m R_D \quad (5.15)$$

### Differential output gain

 

**Figure 5.5:** n-channel MOSFET (NMOS) differential amplifier with a differential output.

The output of a differential amplifier is defined as

$$v_{OD} = v_{out}^+ - v_{out}^- \quad (5.16)$$

For the amplifier in figure 5.5, it can be derived that the single-ended small signal gain observed at node  $v_{out}^-$  is just the negative of the gain observed at the node  $v_{out}^+$ .

$$\frac{v_{out}^-}{v_{in}^+ - v_{in}^-} = -\frac{v_{out}^+}{v_{in}^+ - v_{in}^-} = -\frac{1}{2}g_m R_D \quad (5.17)$$

Therefore, if the output is calculated using equation (5.16)

$$\begin{aligned} v_{od} &= v_{out}^+ - v_{out}^- \\ v_{od} &= \frac{1}{2}g_m R_D v_d - \left(-\frac{1}{2}g_m R_D v_d\right) \\ v_{od} &= g_m R_D v_d \end{aligned}$$




and, therefore,

$$A_d = \frac{v_{od}}{v_d} = g_m R_D \quad (5.18)$$

### 5.4.2 The active load

For a fixed supply voltage, there is an inherent limit on the maximum  $g_m R_D$  that can be built. Increasing  $g_m$  causes the output DC voltage to decrease and eventually the transistor will no longer be in saturation. Increasing  $R_D$  has the same effect, which requires the drain current ( $I_D$ ) to be reduced to have the circuit function correctly. A common solution to this predicament is called an active load circuit, which is a structure that is very similar to a current mirror.<sup>(7)</sup> In section 5.4.1, the resistance  $r_o$  was assumed to be very large to simplify the analysis. Here, we consider what happens when, instead of ignoring it, the very large  $r_o$  of an active load's PMOS replaces  $R_D$  in the original differential amplifier design.

<sup>(7)</sup> Recall an ideal current source has infinite impedance.

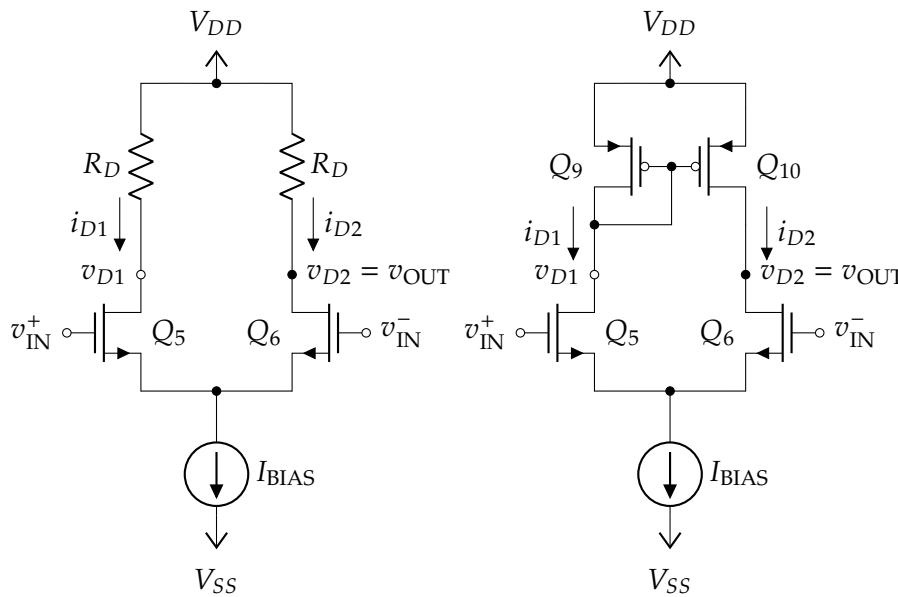

**Figure 5.6:** Comparison of resistive and active loads.

To analyze the active load in figure 5.6, we need to analyze the small signal model again. Unlike the resistively loaded differential amplifier, it is necessary to include the  $r_o$  values for both the NMOS ( $r_{o,n}$ ) and PMOS ( $r_{o,p}$ ) transistors. The value of  $r_o$  is calculated by finding the small signal resistance at the operating point of the transistors. This must be done

using the MOSFET equation with channel length modulation:


$$i_d = \frac{1}{2} k' \frac{W}{L} (v_{GS} - V_{th})^2 (1 + \lambda v_{DS})$$

We want the small signal resistance, so we take the derivative.

As  $\lambda \ll 1$ ,  $i_d$  can be substituted in as an approximation.

$$\frac{1}{r_o} = \frac{\partial i_D}{\partial v_{DS}} = \frac{1}{2} \lambda k' \frac{W}{L} (v_{GS} - V_{th})^2 \approx \lambda i_D \Rightarrow r_o \approx \frac{1}{\lambda i_D}$$

Now that we know all the parameters, it is possible to analyze the small signal circuit using similar techniques used in the previous experiments. Because the NMOS transistors are identical and biased at the same current, they both have the same  $g_{m,n}$  and  $r_{o,n}$ . Similarly, it is also true for the PMOS transistors'  $g_{m,p}$  and  $r_{o,p}$  — this will help simplify our analysis.

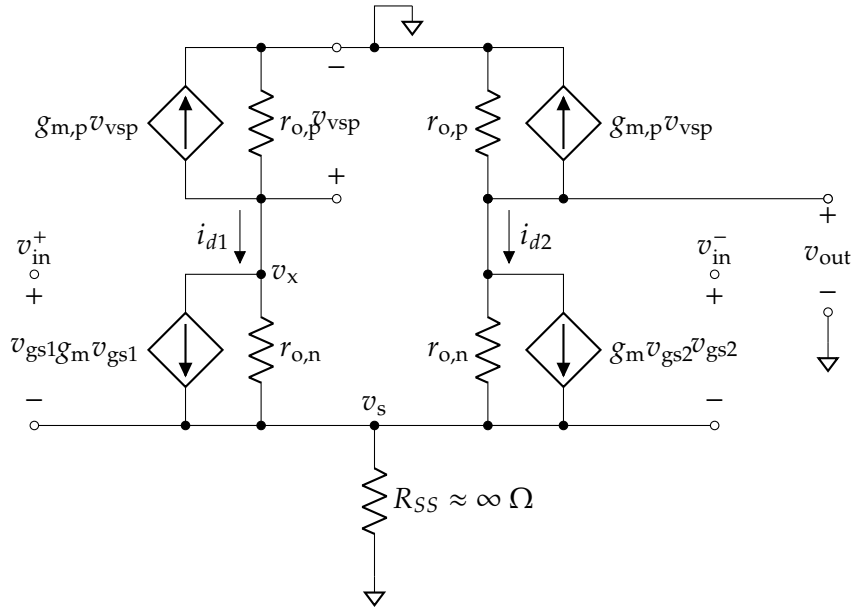

**Figure 5.7:** Small signal model of a differential amplifier with an active load.

Adding the resistances adds a lot of complexity to our circuit equations, but a careful application of nodal analysis and superposition can be used to solve the circuit. First, we assume  $v_{in}^- = 0$ . This results in the following nodal equations:

$$\frac{v_x - v_s}{r_{o,n}} + \frac{v_{out} - v_s}{r_{o,n}} + g_{m,n}(v_{in}^+ - v_s) + g_{m,n}(-v_s) = 0$$

$$\frac{v_x}{r_{o,p}} + g_{m,p}v_x + \frac{v_x - v_s}{r_{o,n}} + g_{m,n}(v_{in}^+ - v_s) = 0$$

$$\frac{v_{out}}{r_{o,p}} + g_{m,p}v_x + \frac{v_{out} - v_s}{r_{o,n}} + g_{m,n}(-v_s) = 0$$

Those equations certainly do not look fun! The equations can be solved<sup>(8)</sup> for  $v_x$ ,  $v_s$ , and  $v_{out}$  in terms of all the parameters that can be calculated from the DC bias. The equation for  $v_{out}$  can be used to find the gain of the circuit

<sup>(8)</sup> We recommend using an equation solver, but you could do it by hand.

$$v_{out} = \frac{g_{m,n} r_{o,n} r_{o,p} (1 + 2g_{m,p} r_{o,p})}{2 (r_{o,n} + r_{o,p}) (1 + g_{m,p} r_{o,p})} v_{in}^+$$

Typically,  $g_{m,p} r_{o,p} \gg 1$ , so we can then simplify by taking the limit:

$$\frac{(1 + 2g_{m,p} r_{o,p})}{2 (1 + g_{m,p} r_{o,p})} \approx 1$$

This simplifies the formula for  $v_{out}$  to:

$$v_{out} = g_{m,n} \frac{r_{o,n} r_{o,p}}{r_{o,n} + r_{o,p}} = g_{m,n} (r_{o,n} \parallel r_{o,p}) v_{in}^+$$


The  $v_{out}$  due to  $v_{in}^-$  is calculated using a similar procedure, which ultimately results in the final equation for  $v_{out}$ . The  $r_o$ 's are significantly larger than the discrete resistors used in the original differential amplifier, so we can expect a huge increase in gain for this circuit. Amazingly, we can get this large increase in gain without increasing power consumption! Unfortunately, it is not all improvements. This method has negative effects on the maximum output swing and linearity.

$$v_{out} = g_{m,n} (r_{o,n} \parallel r_{o,p}) (v_{in}^+ - v_{in}^-) = g_{m,n} (r_{o,n} \parallel r_{o,p}) v_d$$

## 5.5 Ratioed current mirror

In experiment 4, the current mirror was explored. To use less bias current and design multiple stage circuits, we need a current mirror that can have different output currents than input currents. The easiest parameter to control is  $W/L$ . When designing ICs, it is easy to adjust transistor width. Unfortunately, that cannot be done with discrete design; however, it is possible to design current mirrors that have integer multiples of the bias current.

## 5.6 Mirror analysis

 

**Figure 5.8:** Basic MOSFET current mirror.

If  $Q_1$ ,  $Q_2$ , and  $Q_3$  are all the same size of MOSFET, then they will all have the same gate to source voltage ( $V_{GS}$ ) and  $I_D$ . In this case, a simple application of Kirchoff's current law at the drains of  $Q_2$  and  $Q_3$  can be used to determine  $I_O$ :

$$I_O = I_{D,2} + I_{D,3} = 2I_{D,1}$$


## 5.7 Complete differential amplifier circuit

Now that we have both the differential amplifier and the current mirror building blocks, we can put them together to create a working differential amplifier. Taking the amplifier structure of figure 5.3, the ideal current source is replaced with a current mirror. A complete, and realizable, differential amplifier circuit is given in figure 5.9. As we will see in future experiments, this basic circuit structure is used as the front end in a large amount of modern analog circuitry.

**Symmetric output swing** One common starting point when designing a differential amplifier is to aim for maximum symmetric output swing. One method of approximately achieving this requirement is to bias the amplifier such that its output voltage is roughly in the middle of  $V_{DD}$  and  $V_G - V_{th}$  when  $v_d = 0$  V.

$$V_{out,DC} = \frac{V_{DD} + (V_G - V_{th})}{2} \quad (5.19)$$

$V_G$  is the common mode voltage of the input signals. For this experiment, we will use  $V_G = v_{CM} = 0$  V. Biasing for maximum symmetric swing is not always the best choice. There are many trade offs that require consideration when designing a biasing scheme.

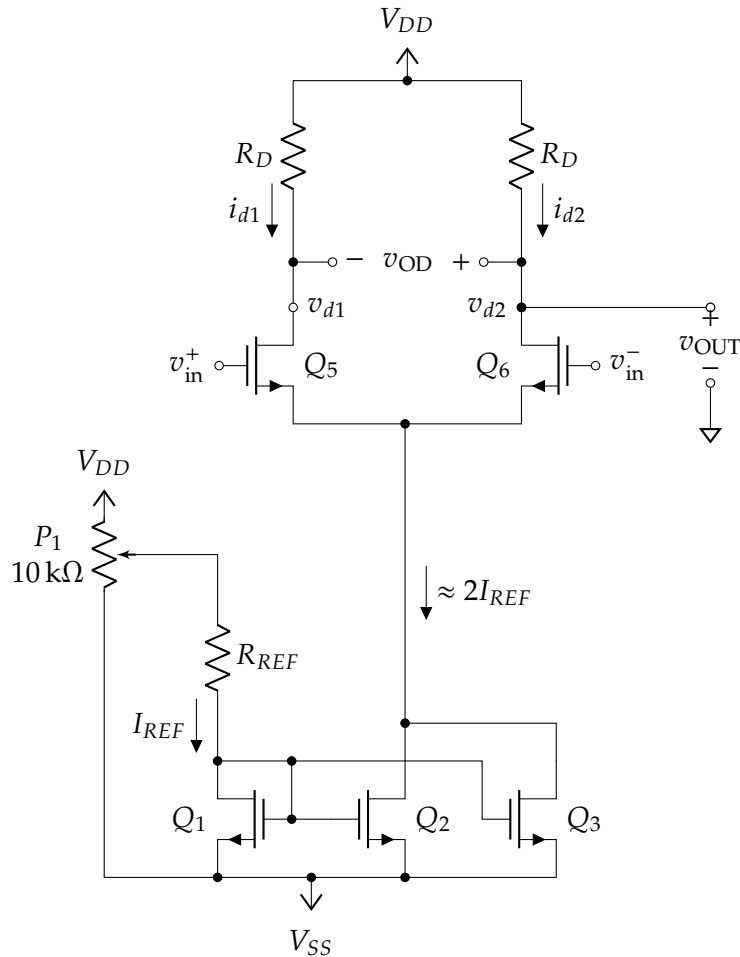

**Figure 5.9:** A MOSFET differential amplifier with current mirror biasing. Note  $Q_{2,3}$  is a “ratioed current mirror” using both  $Q_2$  and  $Q_3$ .

## 5.8 Prelab

### Task 5.8.1: Prelab Questions


1. Calculate  $v_{\text{out}}/v_{\text{in}}^-$  when  $v_{\text{IN}}^+$  is grounded for the circuit in figure 5.4. The procedure is very similar to how  $v_{\text{out}}/v_{\text{in}}^+$  was calculated.
2. Select an  $R_D$  and  $I_{\text{REF}}$  for the circuit in figure 5.9 that results in a single ended gain  $A_v = 4$  and maximum symmetric output swing according to equation (5.19).  $R_D$  should be a standard value that is available to you. What is the expected value of  $I_D$  for each transistor?
3. Calculate the expected gain of the active load differential amplifier in figure 5.6 assuming the NMOS transistors are biased to the same  $I_D$  values from step 2.

## 5.9 Tasks

Please complete the following tasks assuming  $V_{\text{DD}} = 5\text{ V}$  and  $V_{\text{SS}} = -5\text{ V}$ . Use  $V_{\text{TN}} = 0.7\text{ V}$ ,  $k'_n = 32\text{ }\mu\text{A V}^{-2}$ ,  $V_{\text{TP}} = -0.7\text{ V}$ ,  $k'_p = 11\text{ }\mu\text{A V}^{-2}$ ,  $\frac{W}{L} = \frac{138}{7.8}$ ,  $\lambda_n = 0.009$ , and  $\lambda_p = 0.008$ . Use the ALD1106 for  $Q_1$ ,  $Q_2$ , and  $Q_3$ . Use the ALD1105 for  $Q_5$  and  $Q_6$ .

Also recall that  $g_m$  can be computed in terms of  $I_D$  and  $k'$  using the following relationship:

$$g_m = \sqrt{2 \frac{W}{L} k' i_D}$$

 **Task 5.9.1: Build and test the ratioed current mirror****Figure 5.10:** NMOS current mirror with test load.

For this task, use  $V_{DD} = 5\text{ V}$  and  $V_{SS} = -5\text{ V}$ , and use the ALD1106 for the three MOSFETs.


1. Select  $R_{REF}$  and  $R_{TEST}$  so that all transistors stay in saturation over the test range of  $0.1\text{ mA} \leq I_{OUT} \leq 5\text{ mA}$ .
2. Construct<sup>a</sup> the current mirror in figure 5.10 using both  $Q_2$  and  $Q_3$  to create a current doubler.
3. Measure  $I_{REF}$  and  $I_{OUT}$  over the range  $0.1\text{ mA} < I_{OUT} < 5\text{ mA}$ .
4. Plot  $I_{OUT}$  versus  $I_{REF}$  over the test range.
5. Compare the expected and experimental results. Why is the result not a perfect doubler?

<sup>a</sup> You will use this exact current mirror when building the differential amplifier in the next part.

**Task 5.9.2: Build and test the differential pair**

1. Design the circuit from figure 5.11 to achieve a single ended gain of  $A_v = 4$  and approximately symmetric output swing.
2. Construct the circuit from figure 5.11 using the current mirror developed in task 5.9.1 as the current source. Make sure to remove  $R_{TEST}$ . Use the two NMOS transistors in the ALD1105 for  $Q_5$  and  $Q_6$ , and set  $V_{DD} = 5\text{ V}$  and  $V_{SS} = -5\text{ V}$ .


3. Ground both the  $v_{IN}^+$  and  $v_{IN}^-$  inputs and adjust the bias current until  $v_{OUT}$  is at the expected DC value.
4. Measure and record the voltage at  $V_{D5}$  and  $V_{D6}$ . Should they be equal to each other? If they are not as expected, what could be a possible cause of the error?

 

**Figure 5.11:** Differential amplifier connected with a single-ended input.

5. Configure the function generator to supply a 1 kHz sin wave with zero offset and connect it to  $v_{IN}^+$  input. Ground the  $v_{IN}^-$  input. Adjust the amplitude of the  $v_{IN}^+$  input until the output  $v_{OD}$  is 250 mV peak-to-peak. This represents a “single-ended” input and is demonstrated in figure 5.11.  $v_{OD}$  can be measured by using the subtraction feature of your oscilloscope.
  - a) Measure and plot the single-ended output  $v_{OUT}$  and calculate the single ended gain  $A_v$ . Compare with the expected value.
  - b) Measure and plot the differential output  $v_{OD}$  and calculate the differential gain  $A_d$ . Compare with the single-ended value.



 

**Figure 5.12:** Differential amplifier connected with a common mode input.

6. Configure the function generator to have zero offset and  $v_{in} = 250$  mV peak-to-peak amplitude, then connect it to the  $v_{IN}^+$  input. Short the  $v_{IN}^+$  and  $v_{IN}^-$  pins together. This is to ensure that all the applied voltage is common mode and is demonstrated in figure 5.12.
  - a) Compare the nonideal diffamp behavior in equation (5.4) to the ideal behavior in equation (5.18). What is the expected gain of the circuit in figure 5.12 due to a common mode input?
  - b) What do you actually observe?
  - c) Use your observations to compute the common mode gain,  $A_{cm} = \frac{v_{OD}}{v_{CM}}$ .
7. Use your measured values of  $A_d$  and  $A_{cm}$  to compute the amplifiers CMRR in decibels.

### Task 5.9.3: The active load differential amplifier

1. Remove both  $R_D$  resistors from the differential amplifier and replace them with the PMOS active load wired as shown in figure 5.6. Use the two PMOS transistors in the ALD1105.
2. Measure and plot the single-ended input, singled ended output small signal gain.
3. Compare the gain of the active load with the gain of the resistive load.

## 5.10 References

- [1] *INA226 high-side or low-side measurement, bi-directional current and power monitor with I2C compatible interface*, INA226, SBOS547A, Texas Instruments, Aug. 2015. [Online]. Available: <http://www.ti.com/lit/ds/symlink/ina226.pdf>.
- [2] *LMx58-N low-power, dual-operational amplifiers*, LM258, SNOSBT3I, Texas Instruments, Dec. 2014. [Online]. Available: <http://www.ti.com/lit/ds/symlink/lm158-n.pdf>.