

Lab 2 – Notes

Spring 2024

JOHN GERGUIS

General Notes

- Make sure to read the “Lab Report How-To-Guide” before doing the first report.

Format and notes on Write-ups

Header

(should include all the important info, including the number and name of experiment, your name and your partner's name, date, section, serial number of the AD2)


- Abstract: 1 abstract per report that summarizes the tasks in the experiment.
 - List of components/equipment: There should be a subsection including the components and equipment used in the experiment.
- Task 1
 - Objective: Should NOT be a copy of the header of the task
 - Procedure: The steps that you have done in building the circuit and taking measurements. Should be simple and preferably in bullets/steps. Should include the circuit diagram for the circuit built in this task. Must NOT be copied from the manual or any one.
 - Results: Present your results in an easy way to understand. Make sure to have the S/N and time stamp of the AD2 on all the screenshots.
 - Conclusion: Make sure to summarize your findings, compute the errors and comment on the potential sources of errors.
- Task 2
 - Objective
 - Procedure
 - Results
 - Conclusion
- Task 3
 - Objective
 - Procedure
 - Results
 - Conclusion

....

Task 1

Task 2.7.1: RFD3055LE output characteristics

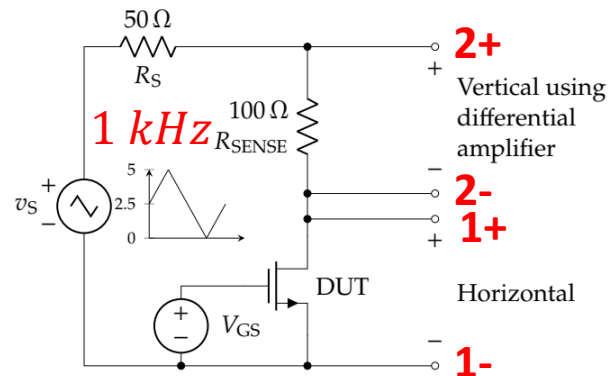1. Select R_{SENSE} for the test set in figure 2.2 to limit the worst case output current to 30 mA. The in lab function generator has a 50 ohm output impedance. The Analog Discovery 2 has a less than 1 ohm output impedance.
2. Construct the test set from figure 2.2 using the R_{SENSE} value calculated in step 1. Note that the diff amp circuit is built into the AD2. A prebuilt diffamp circuit is provided in lab. You will use the prebuilt diff amp circuit in lab or the differential inputs when using the AD2 device to measure measure the voltage across R_{SENSE} .
3. Configure the oscilloscope to use XY mode and plot the I-V characteristic of the RFD3055LE transistor. On the in lab equipment, use persistence to capture one curve in the cut-off region, one curve in the linear region and two curves in the saturation region. On the AD2, capture the 4 curves as separate screenshots.
4. Label the v_{GS} used for each curve.
5. Estimate the power consumed by the transistor for each measured curve at the largest v_{DS} by finding the points using the oscilloscope cursors. Describe the relationship between the power dissipation and transistor's mode of operation.
6. Set $V_{GS} = 5\text{ V}$ then capture an oscilloscope screenshot showing the measurement. Use the results to estimate $R_{DS(on)}$ in the linear region of operation.
7. Compare the computed $R_{DS(on)}$ with the RFD3055LE datasheet $R_{DS(on)}$ value.



1. If you are using the benchtop equipment, then R_s will be $50\ \Omega$ (output impedance of the function generator, you don't need to add it externally). If you are using the AD2, then you will need to add extra $50\ \Omega$, or maybe using R_{sense} to be $150\ \Omega$ instead.
2. Please use the AD2 for this task. Hook up ch1 across V_{ds} and ch2 across R_{sense} . (If you are using the benchtop oscilloscope, you will need to use the diffamp -> Ask a TA)
3. Switch to the mode to the X-Y mode to plot the I-V characteristics. You need to generate 4 curves (1 at cutoff, 2 at saturation, and 1 at the linear region). If you are using the AD2, take screenshots for the 4 curves separately. (If you are using the benchtop oscilloscope, then you will need to use the persistence to show the 4 curves on the same screenshot -> Ask a TA).
5. For each curve, measure V_{DS} and I_{DS} at the very end of each curve, and then compute the power consumption: $P = V_{DS} \cdot I_{DS}$. Comment on the results.

Note: $I_{DS} = \frac{V_{sense} \text{ (voltage from the y-axis)}}{R_{sense}}$

6/7. Set $V_{GS} = 5\text{ v}$, then zoom in (by changing ch1 and ch2 voltage scales). Measure the values of V_{DS} (x-axis) and I_{DS} (y-axis then divide by R_{sense}). $R_{DS} = \frac{\Delta V_{DS}}{\Delta I_{DS}}$. Compare to the value in the datasheet.

Task 2

Task 2.7.2: PWM speed control with MOSFET switch

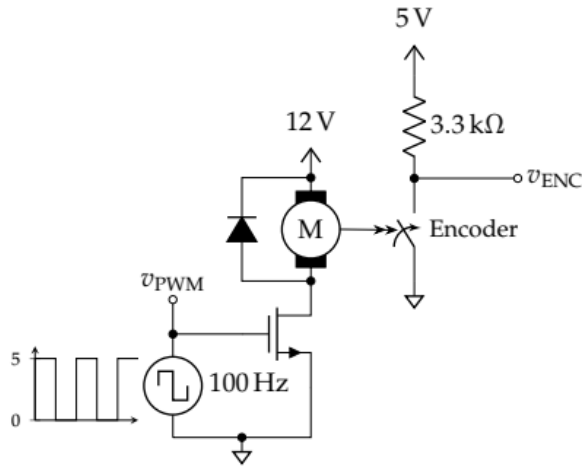


Figure 2.5: PWM motor speed controller.


1. Construct the circuit in figure 2.5. Use either output of the quadrature encoder for v_{ENC} . Use the 1N5819 diode and RFD3055LE MOSFET.
2. Configure the function generator to output a 100 Hz 0 V to 5 V square wave with a duty cycle of 50%.
3. Capture an oscilloscope screenshot showing v_{PWM} and v_{ENC} .
4. Adjust the function generator duty cycle from 10% to 90%. For each step, Record the motor RPM, the encoder frequency, and the average i_D reported by the power supply.
5. Compute the total power consumed by the circuit for each step.
6. Plot the control duty cycle versus the motor RPM and describe the relationship between them.

1. Connect the motor circuit.
 - Make sure to connect M1 to 12v (from benchtop power supply) and M2 to the drain of the Mosfet.
 - Put the diode in the correct orientation.
 - For the encoder part, the 3.3 k is already on the motor (you do not need to add it).
 - Connect the 3.3 v terminal to the power supply (3.3 or 5 v can work), and don't forget to connect the ground terminal. Make sure that a green led lights up.
 - Connect the scope to either C1 or C2 to measure v_{ENC} .
2. The input square wave is ranging between 0-5v (make sure to add offset of 2.5v).

4/5. Sweep the duty cycle (at least 10% step), and measure the corresponding encoder freq, motor RPM and ID (current drawn from the power supply).

- Power = 12v * i_D
- $RPM = \frac{60f}{p*r}$; (p = 11 and r = 34).

6. Plot RPM vs Duty cycle and comment

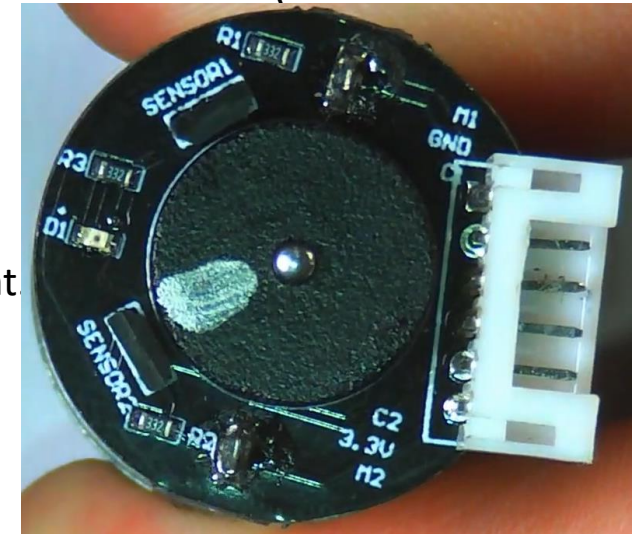

Task 2.7.3: LMC555 based PWM generator


In this task, we will create a circuit that can efficiently control the speed of a motor. Note that any load on the motor will still change the speed as this is open loop control. We will explore controls more in experiment 11.

The circuit diagram shows an LMC555 timer used as a PWM generator. It is powered by a +5V supply connected to its VDD and GND pins. The TRIG pin is connected to a +5V supply through an 8.2 k Ω resistor and also has a 0.1 μ F capacitor connected to ground. The OUT pin of the LMC555 drives the gate of an N-MOSFET. The MOSFET's source is grounded, and its drain is connected to one terminal of a 12V motor supply. The other terminal of the 12V supply is connected to the motor (represented by a circle with 'M') and a diode in parallel. The encoder provides a feedback signal v_{ENC} . The CONT pin of the LMC555 provides the control voltage v_{CTRL} .

Figure 2.6: PWM Modulation Circuit for Motor Speed Control

- Construct the circuit in figure 11.7. Use the 1N5819 for the diode and the RFD3055LE for the NMOS.
- Connect v_{CTRL} to the function generator and configure the function generator to output DC.
- Setup the oscilloscope to measure v_{PWM} and v_{ENC} .
- Adjust v_{CTRL} from 0 V to 5 V and record the duty cycle of v_{PWM} and the speed of the motor at each step.
- Develop a model for the relationship between v_{CTRL} and the speed of the motor.
- Replace the function generator output with a potentiometer circuit that can adjust v_{CTRL} from 0 V to 5 V. Verify that your circuit is able to control the speed of the motor over its full range.

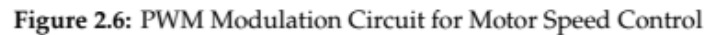In this task, we will create a circuit that can efficiently control the speed of a motor. Note that any load on the motor will still change the speed as this is open loop control. We will explore controls more in experiment 11.



1. Construct the circuit in figure 11.7. Use the 1N5819 for the diode and the RFD3055LE for the NMOS.
2. Connect v_{CTRL} to the function generator and configure the function generator to output DC.
3. Setup the oscilloscope to measure v_{PWM} and v_{ENC} .
4. Adjust v_{CTRL} from 0 V to 5 V and record the duty cycle of v_{PWM} and the speed of the motor at each step.
5. Develop a model for the relationship between v_{CTRL} and the speed of the motor.
6. Replace the function generator output with a potentiometer circuit that can adjust v_{CTRL} from 0 V to 5 V. Verify that your circuit is able to control the speed of the motor over its full range.

To verify that your circuit is working, please report any measurement in your report; show a measured value of vCTRL and its corresponding duty cycle of vPWM and RPM.