

Lab 9.2.2

Tuesday, November 26, 2024

6:37 PM

$$v_C(t) = 1.3e^{-9.2 \times 10^4 t} \sin(7 \times 10^5 t).$$

Underdamped $s = -\sigma + j\omega$ Response: $A \cdot e^{-\sigma t} \sin(\omega t)$ — from lab manual

$\omega / \omega_d \approx 7 \cdot 10^5, \sigma = 9.2 \cdot 10^4$

$\omega_d = \sqrt{\frac{1}{LC} - \sigma^2}, \sigma = \frac{1}{2RC}$

Given: $L = 10^{-3} \text{ H}, C = 2 \cdot 10^{-9} \text{ F}$

$$\sigma = 9.2 \cdot 10^4 = \frac{1}{2R \cdot 2 \cdot 10^{-9}} \Rightarrow R \approx 2717.39 \Omega$$

$$R \approx 2.7 \text{ K}$$

* taking laplace then inverse laplace w/ $R = 2.7 \text{ k}$ to get v_c as funct of t and V

```
untitled0.py x massestim.py x task2.py x
import sympy as sp
import numpy as np
import matplotlib.pyplot as plt

graph = False
# Define symbols
s, v, R, t = sp.symbols('s v R t', positive=True)

# Fixed numeric values for C and L
C = 2e-9 # Capacitance in farads
L = 1e-3 # Inductance in henries

# Uncomment these lines to define numeric values; comment them out to use symbolic coefficients
#v = 4.55 # Example numeric value for input voltage
R = 2700 # Resistance in ohms

# Define symbolic impedance
Z_L = s * L # Impedance of the inductor
Z_C = 1 / (s * C) # Impedance of the capacitor
Z_CL = 1 / (1/Z_L + 1/Z_C) # Parallel combination of Z_L and Z_C
Z_EQ = Z_CL + R # Total impedance

# Define transfer function H(s)
V = v / s # Input voltage in Laplace domain
H_s = V * Z_CL / Z_EQ

# Substitute numeric values for `R` and `v` (already numeric here)
H_s = sp.simplify(H_s)

# Compute the inverse Laplace transform numerically
try:
    h_t = sp.inverse_laplace_transform(H_s, s, t)
```

yields: $(V_{\{c\}}(t)): 0.264165990659424 \cdot v \cdot \exp(-92592.5925925926 \cdot t) \cdot \sin(701018.26780547 \cdot t)$

$$V_c(t) = 0.264165990659424 \cdot v \cdot e^{-92592.5925925926 \cdot t} \cdot \sin(701018.26780547 \cdot t)$$

$$0.264 \cdot v = 1.3 \Rightarrow v \approx 4.92 \text{ V}$$

Plugging in $V = 4.92, R = 2700 \Rightarrow 1.29969667404436 \cdot \exp(-92592.5925925926 \cdot t) \cdot \sin(701018.26780547 \cdot t) \approx v_C(t) = 1.3e^{-9.2 \times 10^4 t} \sin(7 \times 10^5 t).$

$$R = 2.7 \text{ K}\Omega \quad v = 4.92 \text{ V}$$