

# Lab 11 – Notes

## Spring 2024

JOHN GERGUIS

# Task 1

Task 11.4.1: Buck regulator with PWM modulator control

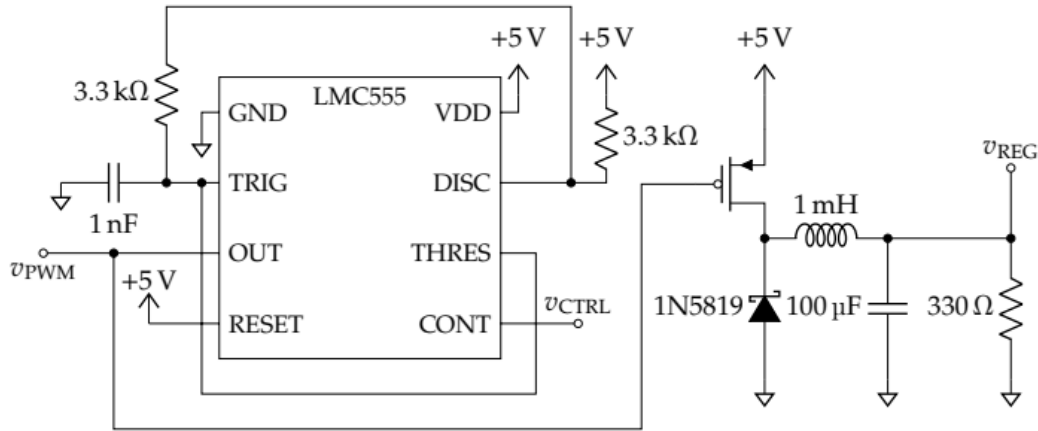


Figure 11.7: PWM Modulation Circuit

1. Construct the circuit in figure 11.7
2. Connect  $v_{CTRL}$  to the function generator and configure the function generator to output DC.
3. Measure and Plot the relationship between  $v_{CTRL}$ , the duty cycle of  $v_{PWM}$ , and  $v_{REG}$ .
4. What control voltage and duty cycle is needed for a 2.5 V output?
5. Change the supply voltage from 5 V to 4 V then *adjust* the control voltage until  $v_{REG} = 2.5$  V. Record the control voltage and PWM duty cycle at this point and compare these values with the answer from step 4.
6. Is this method of controlling the regulated output voltage open loop or closed loop?

**\* Please LEAVE this part built for task 3.**

\* This is the same circuit as lab 10, but you are building a 555-timer circuit to generate the square wave instead of using the function generator.

2. The input is DC voltage (connect the wavegen to Vctrl and configure it to “offset” to generate a DC output).

3. Step up Vctrl from 0-5v (take at least 10 points). Measure the duty cycle of Vpwm and the DC voltage of Vreg at each step. (Note: you can use PosDuty in the AD2 to measure the duty cycle, but if the output of Vpwm looks very distorted, you are encouraged to measure it manually)

Plot 2 curves: Duty\_cycle\_Vpwm vs Vctrl & Vreg vs Vctrl.

5.6./ Change the supply (from 5 to 4v), now ALL the values will change. Why?!!

Re-adjust to get again Vreg = 2.5, record the new values and compare then compare with step 4.

# Task 2

## Task 11.4.2: Error amplifier

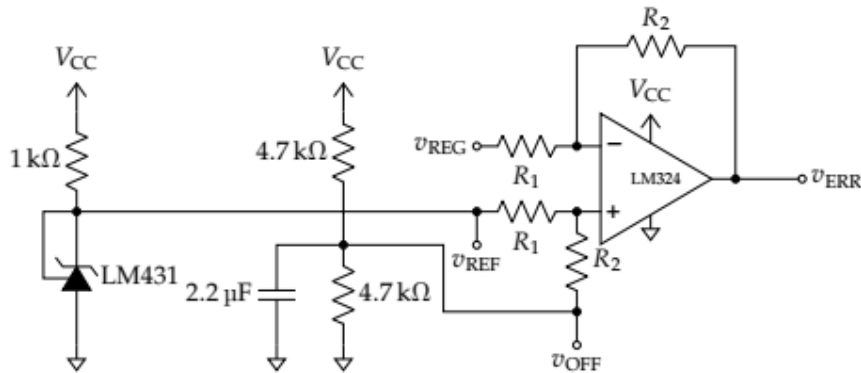


Figure 11.8: PWM Modulation Circuit

In this task, we will design and build an error amplifier that will measure how far from our target voltage of 2.5 V the output of the regulator is. Because this is a single supply design, we must supply an offset voltage to stay within the common mode input and output range of the op amp.

1. Pick  $R_1$  and  $R_2$  in figure 11.8 in order to make  $v_{ERR} = v_{REF} - v_{REG} + v_{OFF}$ . Choose values greater than 20 kΩ.
2. Construct the circuit in figure 11.8 with  $V_{CC} = 5$  V.
3. Connect  $v_{REG}$  to the function generator in DC mode.
4. Sweep the function generator from 1 V to 4 V and record  $v_{ERR}$  at each step.
5. Set  $V_{CC} = 4$  V then repeat step 4.
6. Does the circuit implement the desired error measurement equation? What is the output voltage when the error is zero for each case?

\* Please LEAVE this part built for task 3.

\* Please note the following:

- $v_{REF}$  is always  $\sim 2.5$  v  $\rightarrow$  zener diode  $\rightarrow$  Always constant
- $v_{OFF} = \frac{V_{CC}}{2} \rightarrow$  It changes with the supply
- $v_{REG}$  should be the actual input that we need to compare with (it will be connected to the output of the regulator in task 3). In this task we will be connecting it to the wavegen with an input of DC voltage.

1. Check your values of  $R_1$  &  $R_2$  with a GTA.

4. Take a measurement at every 0.5v step.

5. Change  $V_{CC}=4$ , then sweep again as in step 4.

6. What is meant by the error here is the actual error  $v_{ERR_{actual}} = v_{REF} - v_{REG}$ ,  $v_{OFF}$  is just a DC added to the equation.

What is the output of  $v_{ERR} = v_{REF} - v_{REG} + v_{OFF}$ , when the actual error is zero?!

# Task 3

## Task 11.4.3: Closed loop buck controller

1. Construct the circuit in figure 11.9. Make sure to close the feedback loop by connecting both  $v_{CTRL}$  points together.
2. Set  $V_{CC}$  to 5 V and measure the average value of  $v_{CTRL}$  and  $v_{REG}$ .
3. Sweep  $V_{CC}$  from 4 V to 5 V. Record  $v_{REG}$  and  $v_{CTRL}$  at each step.
4. Capture an oscilloscope screenshot showing  $v_{REG}$  and  $v_{CTRL}$  during the power up sequence. That is, turn off  $V_{CC}$ , set the oscilloscope to single trigger mode, then turn on  $V_{CC} = 5$  V.
5. Replace  $R_L$  with a 150  $\Omega$  resistor. What happens to  $v_{REG}$  and  $v_{CTRL}$ ?
6. Is this control system able to effectively and automatically regulate  $v_{REG}$  over a variety of conditions? What is the relationship between  $V_{CC}$  and the control voltage? What is the relationship between  $R_L$  and the control voltage?
7. Replace the 33 k $\Omega$  resistor in the PI controller with a 2.2 k $\Omega$  resistor while still using  $R_L = 150$   $\Omega$ . What happens to  $v_{CTRL}$  and  $v_{REG}$ ? Obtain an oscilloscope screenshot showing both  $v_{CTRL}$  and  $v_{REG}$  in this configuration. Is the power supply still working correctly?

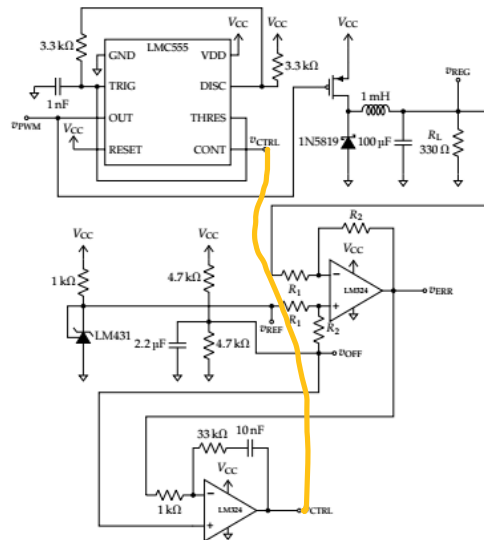


Figure 11.9: Buck Regulator Controller

\* Use the circuits from tasks 1 & 2 to build the whole circuit.

\* Please understand that this circuit is a closed loop, it is built to maintain  $v_{REG}$  to be always at the target value ( $\sim 2.5$  V). For any change in the circuit, any values (e.g.  $v_{CTRL}$  and  $D_{PWM}$ ) can change accordingly to fix  $v_{REG}$ , but  $v_{REG}$  should remain almost constant.

1. Make sure to close the loop (connect  $v_{CTRL}$ ).

3. Here you are changing the supply. (Take at least 10 points)

4. Use “single run” (please check the demo of this part in the video): Turn off the supply -> click single run -> Turn on the supply.

5. Here you are changing  $R_L$ .

6. What are your observations??

7. You need to change the resistance in the PI controller (NOT the load). You should see some oscillations in  $v_{REG}$  or/and  $v_{CTRL}$ .

No oscillations? Try to turn off the supply and turn it on again, or try to remove the load and place it back again.

**Take screenshots and comment on the results.**