Prelab 11


Wednesday, October 23, 2024 21:17

Control loops

open loop - has feedback system

closed - do not 1

Open loop

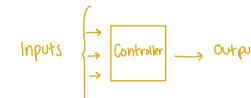

odo not verify motor is in correct state

- require calibration so its correct when it recieves input

otasks that don't require adaption to changing output conditions without user interaction

Closed loop control system

· can ensure it is in correct state instead of

relying on making assumptions

ex. thermostat

freq resp output H(s)_o Control Signal y(t) G(s) error: e(6)= K(t)-y(t) current measured Canstill work well for not def G(s) Feedback system model system will adjust z(t) until the error is minimized

 $\frac{Z(s)}{X(s)} = \frac{H(s)}{1 + G(s)H(s)}$

In simple systems, you only need to have H(s) a large linear gain so sys drives a to minimize

ochanges to the system change y(t)

ochanges in K(t) cause error to 1

loop amp will detect and adjust Z(t)

- requires change in chrl sig


transfer function
$$H(s) = K_p + \frac{1}{s} K_i + s K_d$$

in a syst that needs to quickly change derivitive adds to of system based on a const proportion of the error integrates the


integrates the error geliminates the offset that occurs at the output of a proportional only system ?

Analog control circuits

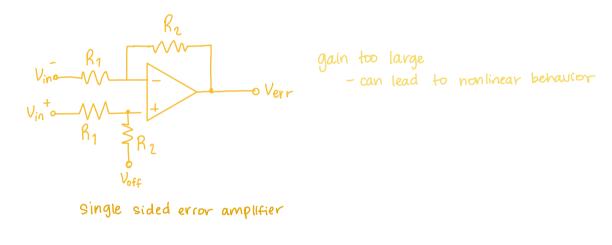Several op amps can make a feedback controller



Error amplifier - drives input of PID

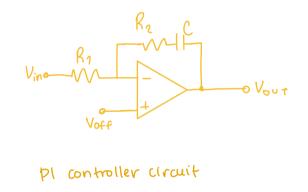

Vout = 11.4 on page 131

1. Open loop - has feedback


dВ


Prelab

Closed loop - doesn't have feedbak

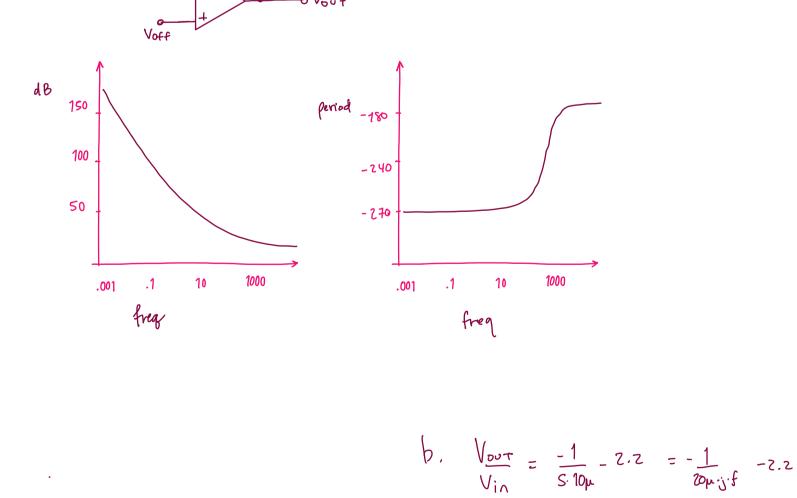2. Magnitude & Phase response

$$\frac{33k}{V_{in}} = \frac{10nF}{V_{in}} = \frac{1}{SR_{1}C} - \frac{R_{2}}{R_{1}} = \frac{1}{S10\mu} - 33 = -\frac{1}{20\mu \cdot j \cdot f} - 33$$



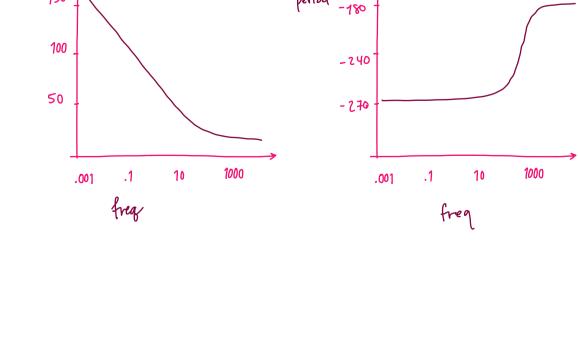

3. a.
$$K_p = \frac{33 \, \text{K} \, \Omega}{1 \, \text{K} \, \Omega} = 33$$
 b. $K_p = \frac{2.2 \, \text{K}}{1 \, \text{K}} = 2.2$

$$K_{i} = \frac{1}{1k \cdot 10nF} = 1 \times 10^{6}$$

$$K_{i} = \frac{1}{1k \cdot 10nF} = 1$$

$$\frac{1}{1k \cdot 10nF} = 1$$

 $R_1 = R_2 = 22 K \Lambda$

$$\frac{V_{ERR} + V_{REG}}{R_2} = \frac{V_{OFF}}{R_2} + \frac{V_{REF}}{R_1} = 0$$

$$R_1 V_{ERR} = R_2 V_{REF} + R_1 V_{OFF} - R_2 V_{REG}$$