

# Lab 3 – Notes

## Spring 2024

JOHN GERGUIS


# General Notes

- Starting from lab 3, you will begin dealing with ALD chips (1105/1106/1107).
- The ALD chips are not in the kit, they will be handed to you with other extra components including the ESD wristband.
- ALD chips are very sensitive to electrostatic charge.
- Please make sure to wear a ESD wristband and connect it to ground before touching any of the ALD chips (check the ESD safety section in the video).
- Don't touch directly the pins of the chips, always try to handle it from the package.

# Task 1

## Task 3.7.1: Determine $V_{tn}$

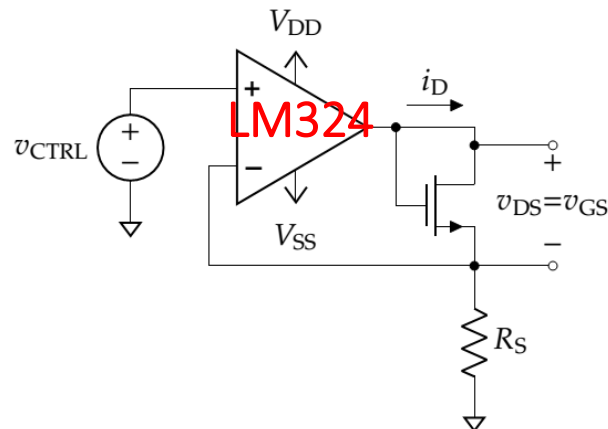1. Connect your ESD wristband to ground and put on the wristband.
2. Place the ALD1106 into your breadboard and connect  $V^-$  to ground and  $V^+$  to  $V_{DD}$ .
3. Build the circuit in figure 3.2 using  $R_S = 100\text{ k}\Omega$ ,  $V_{DD} = 5\text{ V}$ , and  $V_{SS} = -5\text{ V}$ . Use any of the four transistors on the ALD1106.
4. Set  $v_{CTRL}$  to the value calculated in prelab step 4.
5. Measure the voltage across  $R_S$  to ensure that  $i_D$  is set to  $1\text{ }\mu\text{A}$ .
6. Measure  $v_{GS}$ . This is the threshold voltage of the transistor.
7. Repeat the threshold voltage measurement for all four transistors on the ALD1106.
8. Compare the threshold voltages of the four measured transistors. Do the transistors have similar threshold voltages?
9. Compare the threshold voltages to the range listed on the ALD1106 datasheet. Does your measurement fall within the range listed on the datasheet?



\*  $V^-$  is connected to ground in this task.

\* The opamp chip is LM324.


4. Check the value of  $V_{ctrl}$  with a GTA.

5/6 Measure the voltages using the voltmeter tool.

7. Measure  $V_{gs}$  ( $V_{th}$ ) for all the 4 transistors.

# Task 2

### Task 3.7.2: Estimate $k_n$

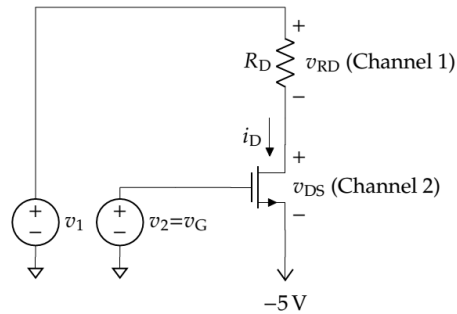

**Figure 3.4:** Test set for measuring the drain characteristics.

1. Place the ALD1106 in your breadboard and connect  $V^-$  to  $V_{SS}$  and  $V^+$  to  $V_{DD}$ .
2. Set up the to measure the drain I-V characteristics of the transistor by building the circuit in figure 3.4 with  $R_D = 470\ \Omega$ . Use W1 to generate  $v_1$  and W2 to generate  $v_2$ . Use the oscilloscope channel 1 to measure  $v_{DS}$  and channel 2 to measured  $v_{RD}$ . Make sure to connect the source of the NMOS in the ALD1106 to  $V_{SS}$ .
3. Set the power supplies to  $V_{DD} = 5\text{ V}$  and  $V_{SS} = -5\text{ V}$  then turn them on.
4. Open the “Tracer” tool in Waveforms<sup>a</sup>.
5. Set the device to “N-FET” and change the adapter dropdown to “No Adapter.”
6. Open the options dropdown and change “Emitter” to  $-5\text{ V}$ .
7. Ensure that “Measure” is set to “Id/Vds”
8. Configure the curve tracer to measure from  $v_{GS} = 0\text{ V}$  to  $v_{GS} = 5\text{ V}$  in even  $500\text{ mV}$  steps over the range  $0\text{ V} \leq v_{RD} < 10$ .
9. Set  $R_D = 470\ \Omega$  in the tracer tool.
10. Run the curve tracer and save a screenshot of the output.
11. Calculate the  $k_n$  value for each curve that the transistor enters saturation. Use the  $V_m$  measured in task 3.7.1.

<sup>a</sup> If you can't find this tool, you need to update to the newest version of waveforms.


\* V- is connected to -5v in this task.

\* Check the demo on the curve tracer tool in the video for this task.

2->10 Follow the instruction to plot the I-V characteristics for 11 curves.

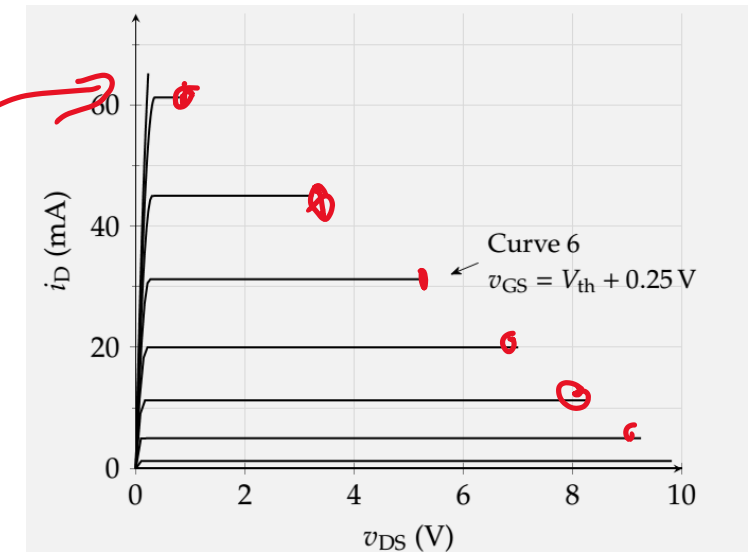11. Compute  $K_n$  for all curves. Use  $V_{th}$  from task 1. get  $I_d$  and  $V_{gs}$  values from the curves.

$$k_n = \frac{2i_D}{(v_{GS} - V_{th})^2}$$



# Task 3

## Task 3.7.3: Estimate $g_m$

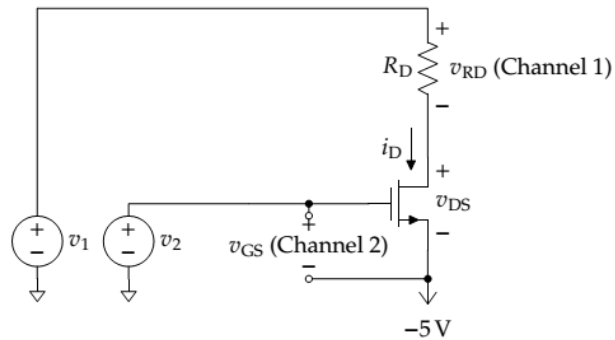


Figure 3.5: Test set for measuring the  $i_D$  vs.  $v_{GS}$  characteristics.

1. Construct the circuit in figure 3.5. This is almost the same circuit as task 3.7.2, except channel 2 is now measuring  $v_{GS}$ .
2. Configure the tracer tool in Waveforms to measure " $i_D/v_{GS}$ ."
3. Set the drain voltage to a constant 5 V
4. Configure the gate voltage to sweep from 0 V to 5 V in 100 mV steps.
5. Run the curve tracer.
6. Capture a screenshot of the curve tracer output.
7. Export the data from the curve tracer and load it into MATLAB, Excel, or a similar tool.
8. Calculate  $g_m$  for each point using equation (3.5).
9. Plot  $g_m$  vs.  $i_D$ . What is the correlation between  $i_D$  and  $g_m$ ?
10. Plot  $g_m$  vs.  $v_{GS}$  and your answer to prelab question 2. Use the  $V_{th}$  you measured in task 3.7.1 and the  $k_n$  you calculated for the curve corresponding to  $v_{GS} = 2.5$  V in task 3.7.2. Over what range of voltages does the model agree with the measurement?

\* V- is connected to -5v in this task.

\* Check the video on how to export data and compute  $g_m$  using excel or Matlab.

\* Make sure to put the steps of  $V_{rd}$ : 1 in the settings, to get only 1 curve for  $I_d$  vs  $V_{gs}$

6. Take screenshot for  $I_d$ - $V_{gs}$

9. Plot  $g_m$  vs  $I_d$  from the measured data (using excel for example) + comment on correlation.

10. Draw 2 curves for  $g_m$  vs  $V_{gs}$  on the same plot:

a) Curve 1: From measured data (using excel for example).

b) Curve 2: From the theoretical relation  $g_m = K_n(V_{gs} - V_{th})$ . Use  $V_{th}$  from task 1, and  $K_n$  from task 2 for the curve corresponding to  $v_{gs} = 2.5$ v.

Comment on the range of agreement between the 2 curves

