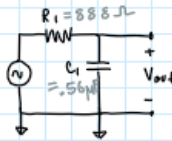


### Low Pass filter



• Cutoff @ 320 Hz  $\pm 10\%$

$$F_c = \frac{1}{2\pi R_1 C_1} \quad C_1 = 0.56 \mu F$$


$$(2\pi \cdot 56 \mu F) 320 = \frac{1}{2\pi R_1 (0.56 \mu F)}$$

$$0.00126 = \frac{1}{R_1}$$

$$R_1 = 888 \Omega$$

Procedure: build circuit in figure X. Use Y components. Check by doing Z

### Mid Pass filter

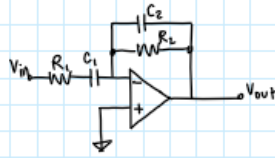

• bandwidth 320 Hz  $\rightarrow$  3200 Hz  $\pm 10\%$


$$F_{c1} = \frac{1}{2\pi R_1 C_1} \quad F_{c2} = \frac{1}{2\pi R_2 C_2}$$

$$C_1 = 10 \mu F \quad C_2 = 1 \mu F$$

$$320 = \frac{1}{2\pi R_1 10 \mu F} \quad 3200 = \frac{1}{2\pi R_2 1 \mu F}$$

$$R_1 = 497 \Omega \quad R_2 = 49.7 \Omega$$

### High Pass filter

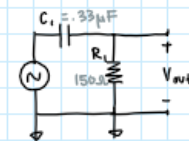

• cutoff @ 3200 Hz  $\pm 10\%$


$$F_c = \frac{1}{2\pi R_1 C_1}$$

$$(2\pi \cdot 33 \mu F) 3200 = \frac{1}{2\pi R_1 (0.33 \mu F)}$$

$$0.00664 = \frac{1}{R_1}$$

$$R_1 = 150 \Omega$$

### Volume control - LM356

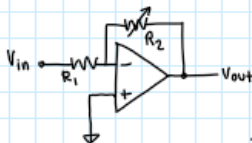

• attach  $V_{in}$  to output  
•  $V_{out}$  to signal recombination

$R_2 \rightarrow 10K$  pot  
find  $R_1$  off of  $R_2$   
• starting @ 10k for max gain of 2  
• to get  $R_1$ , adjusted  $\Omega$  until voltage max  
output is equal across all 3

Low Pass:  $R_1: 20k\Omega$   
Mid Pass:  $R_1: 11k\Omega$   
High Pass:  $R_1: 9.1k\Omega$

### Abstract

- audio technology
- created audio equalizer
- simulated in SPICE
- circuit created
- measured outputs
- played music
- used passive & active filters
- High & low
- mid
- created audio amplifier - calculated


### Objective

- create analog audio equalizer & amplifier
- freq range:  $\leq 320$  Hz,  $320$  Hz -  $3200$  Hz,  $\geq 3200$  Hz
- overall volume control
- amplifier to make it able to drive speakers
- tested through oscilloscope & playing audio


### Conclusion

- Experiment completed objectives
- Graphs & demo were successful
- Audio produced was clean

### Summation op amp - adjustable gain

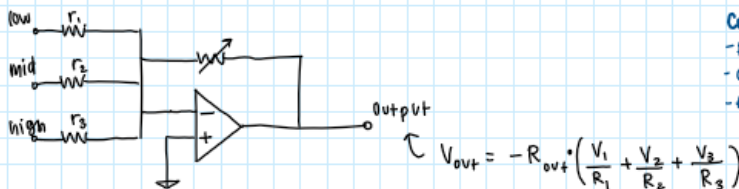


### Amplification

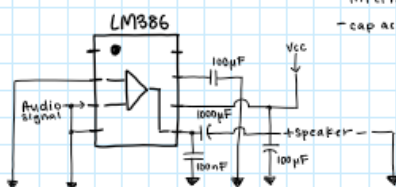

- internal Gain: 20  
- cap across 1 & 8 will increase gain

## Equalizer

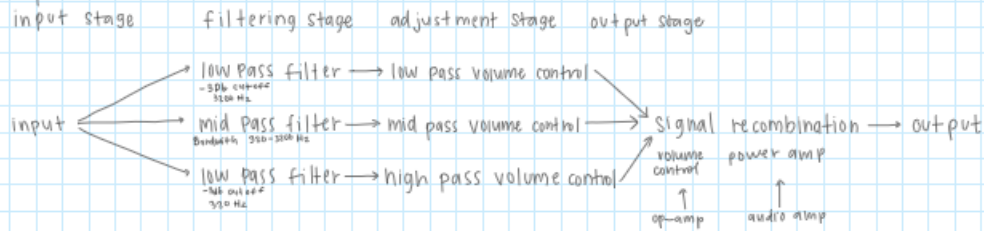

## Power amp

- we use class AB amp → low power multistage transistor amp
- more current than op-amps

## Quick Review - Passive filters

- Lab 8

## Active filtering

- involves op-amp component
  - controllable gain
  - better output isolation
  - higher-order cutoff rate

## Buffering

- most important part of this project
  - o terminal impedances: another form of loading
- view this project as input loading
  - back end of circuit begins to effect the front end
  - o if you try to change the cutoff of 1 filter, it likely will change the cutoffs of the other 2
  - get around this by creating voltage followers through buffer implementation

Buffers isolate an input signal from output signal

- takes input signal → electrically recreates it on the output
  - 2 separate circuits

\* if you can't get cutoffs right, try putting a buffer before input of filter

## Volume control

- reliably reduce amplitude of outgoing waveform
- use op-amp & resistor
  - op-amps carry an isolation property
    - \* less intense than buffer

## Signal Recombination

- summation amplifiers → normal inverting amps w/ multiple inputs on negative terminal
  - basic & add signals to 1 combined



High pass & low pass  
- similar - just cap/resistor placement

Mid pass  $\rightarrow$  RLC filter  $\rightarrow$  better sound/harder to calculate  
 $\rightarrow$  High pass + buffer + low pass - easier to calculate/sounds "finer"

• E equations in lab manual

3/4 circuits  $\rightarrow$  all work in par

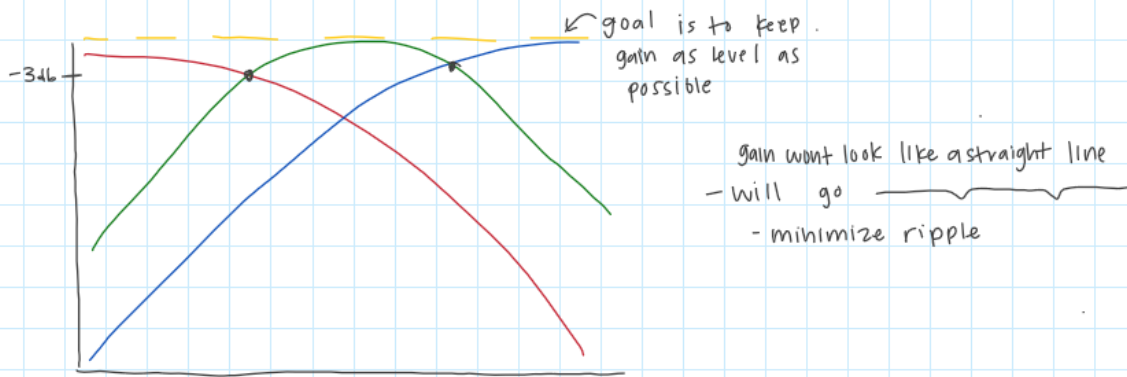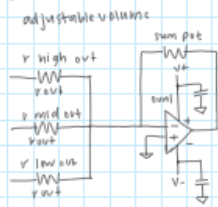Adjust volume  $\rightarrow$  op amp w/ adjustable gain - use pot to adjust gain  
 $\rightarrow$  modified amplifier like in op-amp lab



High pass - cutoff @ 3200 Hz  $\pm 10\%$

Mid pass - bandwidth from 320 Hz - 3200 Hz  $\pm 10\%$

Low pass - cutoff @ 320 Hz  $\pm 10\%$

factor of 10 - easily changed by  
changing cap by factor of 10